



3

**VEERMATA JIJABAI TECHNOLOGICAL INSTITUTE**  
 [Central Technological Institute, Maharashtra State]  
 Matunga, Mumbai-400 019

SEMESTER EXAMINATION	May 2009	DATE OF EXAM	7 <sup>th</sup> May 2009
SEMESTER & COURSE	IV S Y B Tech Eletrix	TIME	2.30 p.m. To 5.30 p.m.
TIME ALLOWED	3 HRS.	MARKS	100
SUBJECT :	<b>ELECTRICAL NETWORK ANALYSIS</b>		

- Instructions:
1. Attempt Any Five Questions.
  2. Figures to the right indicate Full Marks.
  3. Assume suitable **additional data**, if required.
  4. Illustrate your answer with neat sketches whenever necessary.

Q1. a) Replace the network of Fig Q1 (a) at terminal a-b with a Norton's equivalent and Thevenin's Equivalent network. (10)

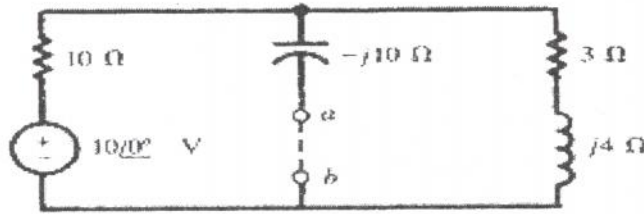


Fig Q1 (a)

b) Determine the voltage across 20 ohm resistor in the following circuit with the help of Superposition theorem. (Fig Q1 (b)) (10)

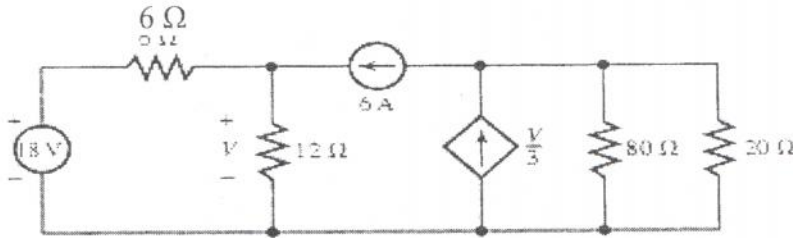


Fig Q1 (b)

Q2 (a) For the circuit shown in Fig Q2(a) draw oriented graph and write i) Incidence matrix, ii) Fundamental cutset matrix, iii) Tie set matrix. (10)

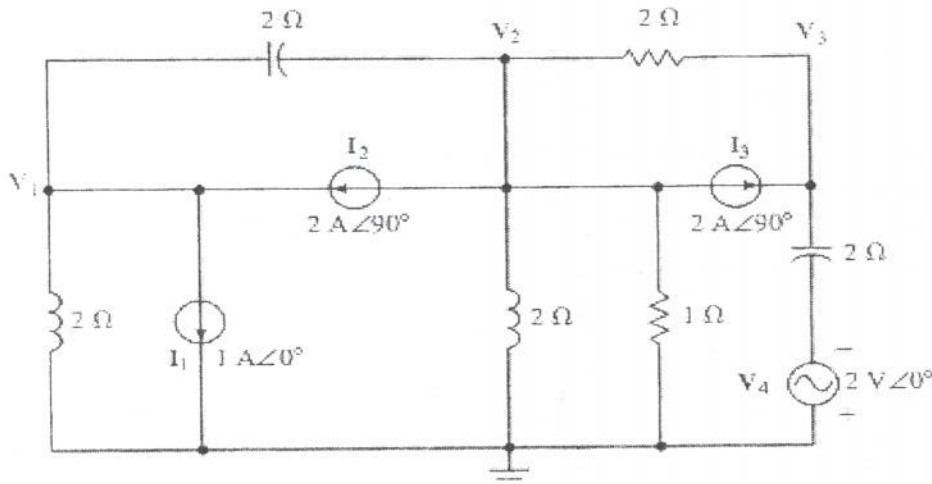


Fig Q2 (a)

b) For the network shown prove that  $AB^T = 0$ .

(10)

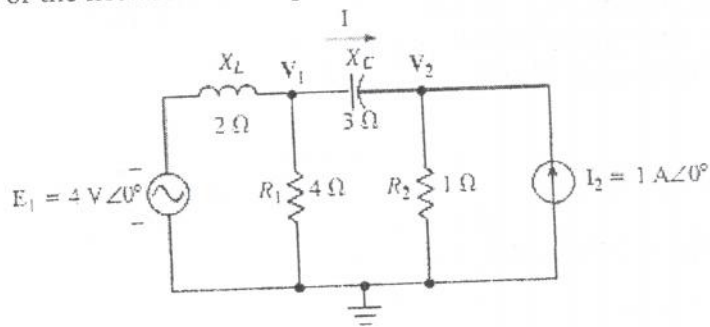


Fig Q2 (b)

Q3 a) Determine  $i_L(t)$  for  $t > 0$ . the circuit of Fig Q3 (a).

(10)

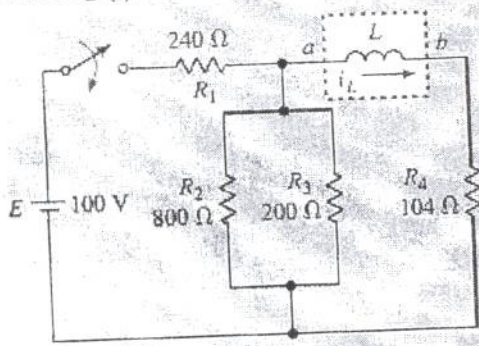


Fig Q3 (a)

b) Find  $i$ ,  $di/dt$ ,  $di^2/dt^2$  for the network shown in Fig Q3 (b).

(10)

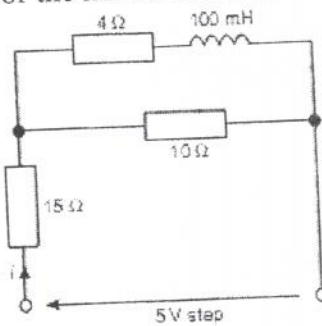


Fig Q3 (b)

Q4 a) For the circuit shown find  $i(t)$  for  $t > 0$  using Laplace Transform. The switch is closed at  $t = 0$ .

(10)

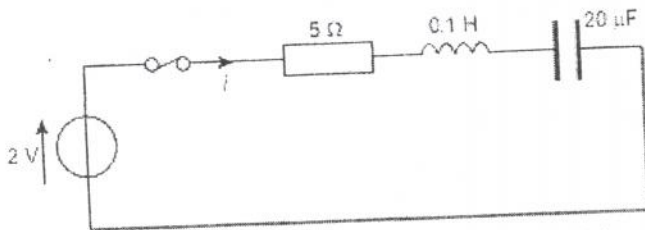


Fig Q4 (a)

b) In the R-L circuit shown the switch is in position 1 long enough to establish steady state conditions, and at  $t = 0$  it is in position 2, Find  $i(t)$  for  $t > 0$  using Laplace transform.

(10)

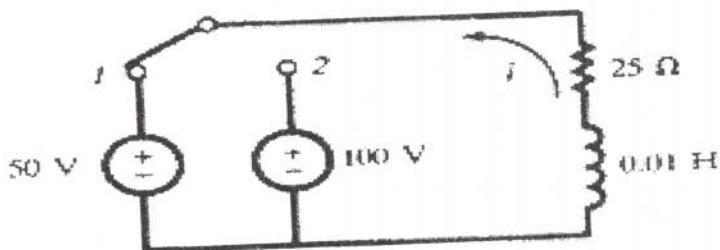


Fig. Q4 (b)